

L6: Muxes and other Components

18-240: Structure and Design of Digital Systems

Bill Nace & Saugata Ghose
Spring 2019

© 2004 - 2019 All Rights Reserved. All work contained herein is copyrighted and used by permission of the authors. Contact ece240-staff@lists.andrew.cmu.edu for permission or for more information.



Electrical & Computer
ENGINEERING


Carnegie Mellon University

18-240: Where are we...?

Carnegie Mellon

- 1 Handout: Lecture Notes
- Midterm 1 -- the countdown begins

Week	Date	Lecture	Reading	Lab	HW
3	1/29	L4 Automated Logic Minimization		Lab 1	HW 2
	1/31	L5 Synthesizable SystemVerilog	LDVUS 2 - 2.3 HH 4.2-4.3		
	2/1	R2 Recitation			
4	2/5	L6 Combinational Components	HH 2.8, 4.5	Lab 2	HW 3
	2/7	L7 Numbers and Arithmetic	HH 1.4, 5.1-5.3		
	2.8	R3 Recitation			
5	2/12	L8 Comb. Logic Wrap-up	LDVUS 2.7 HH 1.7, 2.5-2.6	Lab 3	HW 4
	2/14	L9 Flip-flops and FSMs	HH 3.4		
	2/15	R4 Recitation			
	2/19	Midterm 1		No Lab	HW 5
	2/21	L10 FSM Design	LDVUS 3 - 3.3 HH 3.4, 4.4		
	2/22	R5 Recitation			

 

Today: Structured Logic Realization

Carnegie Mellon


- **What you know so far...**
 - Kmaps and 2-level SOP for smallish (random) logic functions
 - QM can be used too — or a computer tool based on QM
- **What you don't know...**
 - Other ways to approach large designs
 - Partitioning a design into smaller, more manageable chunks
 - Using **pre-designed components**
 - ◆ as parts of larger designs
 - ◆ as configurable devices
- **Today**
 - Multiplexers (and factoring big Boolean expressions)
 - Decoders (and more factoring...)
 - Other useful combinational components: Comparators, Demultiplexers

Multiplexers

Multiplexers (aka Mux)

Carnegie Mellon

 - Consider 1-bit 2:1 Multiplexer
 - Truth table is given
 - Can you write Boolean equation for output?




S	I_1	I_0	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Mission:


Multiplexers: Drawing Conventions

Carnegie Mellon


Normal

 

Plain

 

Minimalist

 

- Specifications


- Size: how many **different** inputs (2^n) can be selected?
- Bit-Width: how many bits wide is **each** input?

- In general

- 2^n data inputs, n **select** lines (also called control inputs), 1 output
 - ♦ a $2^n:1$ or “ 2^n by 1” mux
- Select lines form binary index used to choose (select) an input

Multiplexers: Example usage

Carnegie Mellon

 

A shared “functional unit,” in this case, a binary adder

Depending on Sa and Sb, we can add:
 $A0+B0$, $A0+B1$, $A1+B0$, or $A1+B1$


If inputs (A0...B1) are 16-bit variables, then the muxes are 16-bit, 2:1 muxes

Multiplexers: Gate-level

Carnegie Mellon


- What's inside the Mux? gate-level implementation?
 - All Muxes have a very stylized, easy to recognize form

$$F = S' I_0 + S I_1$$

 

Gate Level
Implementation
of 2:1 Mux

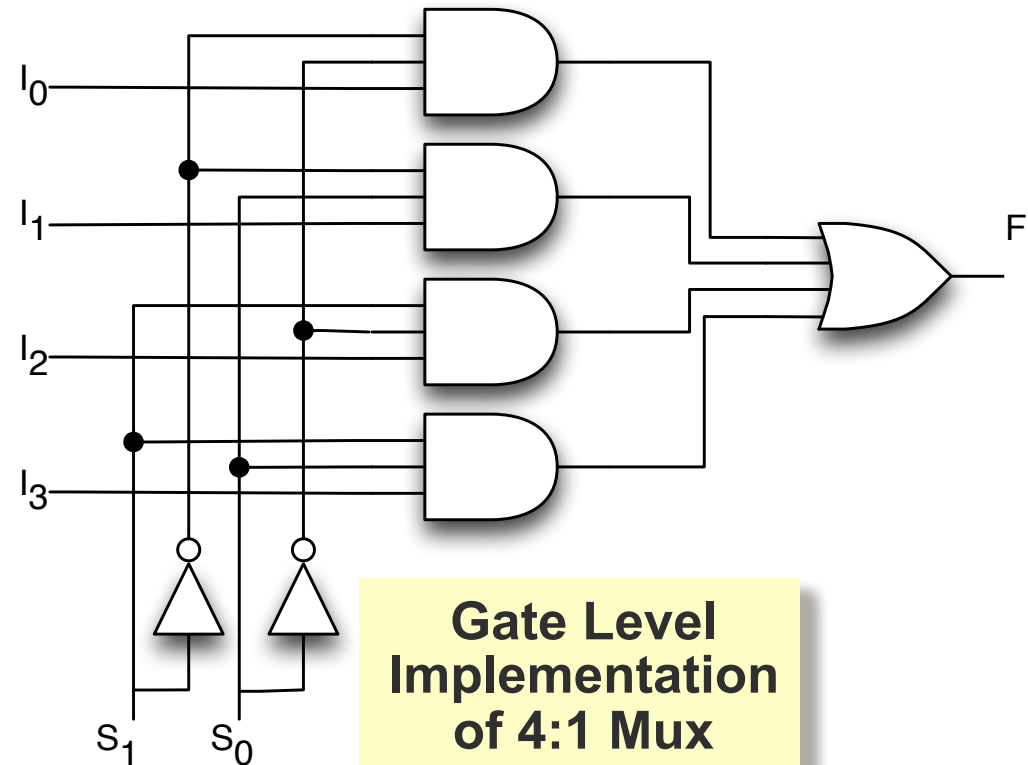
$$F = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$




Gate Level
Implementation
of 4:1 Mux

Multiplexers: Ditto for Bigger Ones...

Carnegie Mellon

 


$$F = S' I_0 + S I_1$$

 

$$F = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

Whoa! There's a minterm expansion in each of these expressions

 The minterms of the *select* input(s) are generated



$$1 \cdot I_5$$

$$F = S_2' S_1' S_0' I_0 + S_2' S_1' S_0 I_1 + S_2' S_1 S_0' I_2 + S_2' S_1 S_0 I_3 + S_2 S_1' S_0' I_4 + S_2 S_1' S_0 I_5 + S_2 S_1 S_0' I_6 + S_2 S_1 S_0 I_7$$

Multiplexers: Use as Logic

Carnegie Mellon

- $2^n:1$ mux can implement n-variable function (easy)
 - Just a lookup table; put TT row k value on k-th mux input


Example: $F(A,B,C) = m_0 + m_2 + m_6 + m_7$

$$= A' B' C' + A' B C' + A B C' + A B C$$

$$= A' B' C' (1) + A' B' C (0) + A' B C' (1) + A' B C (0) \\ + A B' C' (0) + A B' C (0) + A B C' (1) + A B C (1)$$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

“Lookup Table”

 


Put Functions on the Inputs

Carnegie Mellon

- $2^{n-1}:1$ mux can implement n-variable function (subtle)
 - Still a lookup table; but each mux input is now a *function*

Example: $F(A,B,C) = m_0 + m_2 + m_6 + m_7$
 $= A' B' C' + A' B C' + A B C' + A B C$
 $= \boxed{A' B'} (C') + \boxed{A' B} (C') + \boxed{A B'} (0) + \boxed{A B} (1)$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


Why is this useful?

Carnegie Mellon

- **Big functions**

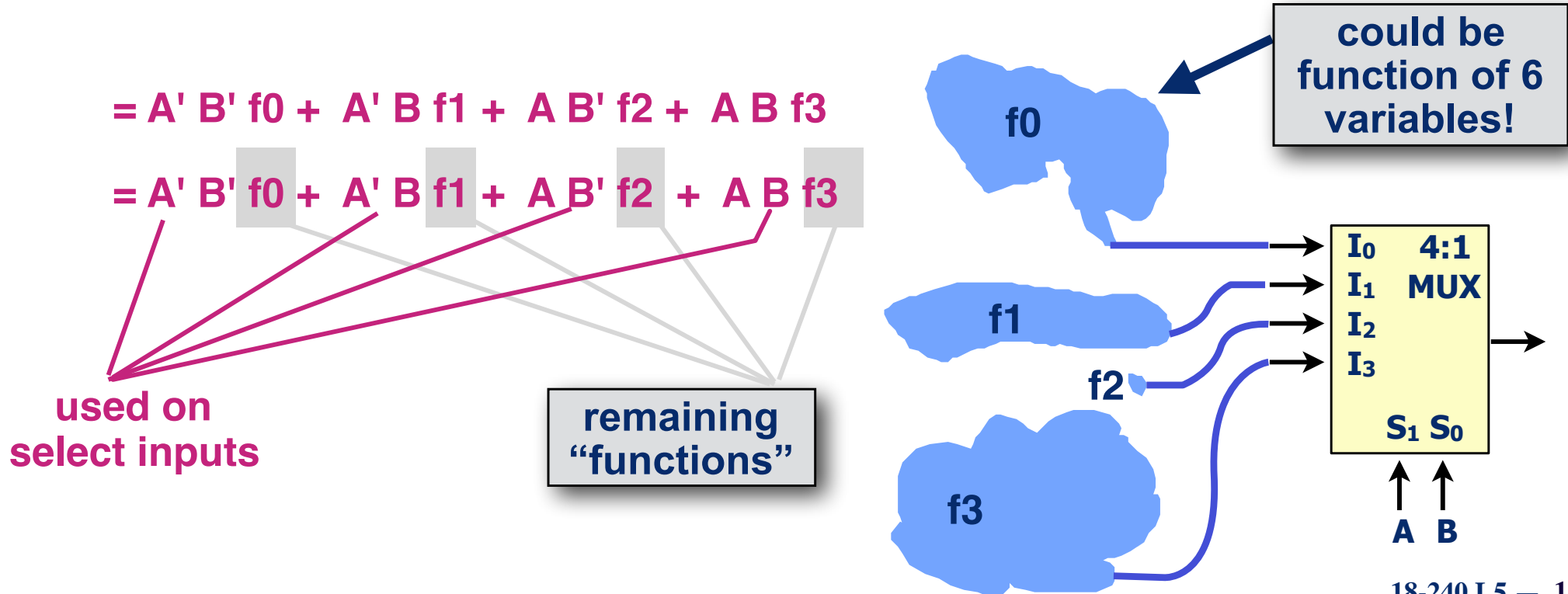- Input C from the previous slide could be a bigger function
- Suggests a method for implementing functions of many variables
- That is, **factor** the function so that
 - ✦ some of the variables are select inputs to a mux
 - ✦ the remaining functions are data inputs to the mux



Shannon Expansion

Carnegie Mellon

- So, how do we *factor* the eqn?
 - Suppose we have a function $F(x_1, x_2, \dots, x_n)$
 - We define a new function if we set one of the $x_i = \text{constant}$
 - Example: $F(x_1, x_2, \dots, x_i=1, \dots, x_n)$
 - Example: $F(x_1, x_2, \dots, x_i=0, \dots, x_n)$
- Easy to do by hand

$$F(a,b,c) = ab + ac' + b(a'c + c')$$


$$F(a=1,b,c) =$$

$$F(a=0,b,c) =$$

- Important to remember that result is a *new function*
 - Note that new function no longer depends on chosen variable

Shannon Expansion

Carnegie Mellon

 

- Turns out to be incredibly useful idea
 - These new functions are called **Shannon cofactors** (or just cofactors) of the original function
 - Shannon Cofactor with respect to x_i
 - ✦ Write $F(x_1, x_2, \dots, x_i=1, \dots, x_n)$ as F_{x_i}
 - ✦ Write $F(x_1, x_2, \dots, x_i=0, \dots, x_n)$ as $F_{x_i'}$
 - ✦ Also can write as just $F(x_i=1)$ $F(x_i=0)$ (which is easier to type)
- Shannon Expansion Theorem
 - Given any Boolean function $F(x_1, x_2, \dots, x_n)$ and any x_i in the variables $F()$ depends on,

$F()$ can be represented as

$F(x_1, x_2, \dots, x_n) =$

What this looks like

Carnegie Mellon



- For $F(a,b,c) = ab + ac' + b(a'c + c')$

$$F(a=0) = F_{a'} = b$$

$$F(a=1) = F_a = b + c' + bc' \\ = b + c'$$

Putting it back

 
 
$$\begin{aligned} F &= a'F_{a'} + aF_a \\ &= a'(b) + a(b+c') \\ &= a'b + ab + ac' \\ &= b + ac' \quad (\text{min sop}) \\ &= b(1+c') + ac' \\ &= b + bc' + ac' \\ &= b(a+a') + bc' + ac' \\ &= ab + a'b + bc' + ac' \\ &= ab + ac' + b(a' + c') \\ &= ab + ac' + b(a'c + c') \end{aligned}$$



Another view

Carnegie Mellon

  - Cofactors of this 5-variable function
 - Clearly, it's important to pick the variable to cofactor around. Why? (What if all prime implicants are independent of the chosen variable)
 - If we chose A, then draw kmap with A as the first variable so F_A and $F_{A'}$ are the top and bottom Kmaps



Which variable to factor?

Carnegie Mellon


- The factoring variables affect complexity
 - A heuristic: pick a variable that shows up a lot in both true and complement form to zero out product terms in the expansion
- Example...

$$F = b + a'c'd + acd'$$

If you pick **a** to factor around:

$F_a =$

$F_{a'} =$

 

Which variable to factor?

Carnegie Mellon


- Same example...

$$F = b + a'c'd + acd'$$

If you pick **b** to factor around:

$F_b =$

$F_{b'} =$

 

Advanced Boolean Algebra

Carnegie Mellon

- You can do this for more than one variable at a time
 - Shannon Cofactor with respect to x_i and x_j
 - ✦ Write $F(x_1, x_2, \dots, x_i=1, \dots, x_j=0, \dots, x_n)$ as $F_{x_i x_j'}$
 - ✦ Ditto for any number of variables x_i, x_j, x_k, \dots
 - Now, the expansion is around the 4 combinations of the 2 variables
 - ✦ Before we wrote:
$$F(x_1, x_2, \dots, x_n) = x_i \cdot F_{x_i} + x_i' \cdot F_{x_i'}$$
 - ✦ Now, we can write:
$$F(x,y,z,w) =$$
 - ✦ Note that $F_{xy} = F(x=1, y=1, z, w)$ is a Boolean function of z and w
 - We've removed 2 variables
 - ✦ could remove even more

Cofactor Summary

Carnegie Mellon

- Why is this cool?
 - We have taken a *big* function and factored it into *smaller* ones
 - The standard engineering approach of divide and conquer
- These examples are way too small
 - You only get some feel of how the Boolean functions split up
 - And, what you might do if confronted with:
 - ♦ a **big** function, especially when good factorization exist
 - ♦ no CAD tools
- Left to another course (18-760)
 - Detail, insight, expansion about what we just did
 - ♦ A recursive approach that just keeps factoring the remaining functions until the resulting cofactor is something reasonable
 - ♦ Which variables do you expand around?

2:1 Mux: SystemVerilog

Carnegie Mellon

- You've seen this before

```
module multiplexer
  (input  logic sel, i0, i1,
   output logic f);

  assign f = (sel) ? i1 : i0;

endmodule : multiplexer
```

```
module multiplexer
  (input  logic sel, i0, i1,
   output logic f);

  always_comb begin
    f = i0;
    if (sel)
      f = i1;
  end

endmodule : multiplexer
```

- Also, multi-bit mux

```
module multiplexer
  (input  logic      sel,
   input  logic [7:0] i0, i1,
   output logic [7:0] f);

  assign f = (sel) ? i1 : i0;

endmodule : multiplexer
```

Still 2:1, just
bigger sized
items to choose
from



2^{sel}:1 Mux: SystemVerilog


Carnegie Mellon

- Choice can also be over more inputs

```
module multiplexer_4to1
  (input  logic [1:0] sel,
   input  logic [3:0] i,
   output logic f);

  always_comb
    case (sel)
      2'b00 : f = i[0];
      2'b01 : f = i[1];
      2'b10 : f = i[2];
      default : f = i[3];
    endcase

endmodule : multiplexer_4to1
```

 


Gonna get
tiring for many
inputs

There must be a
better way!

Standard Components

Carnegie Mellon

- **Mux is an example of a standard component**
 - Used to make bigger designs
- **Historically, available as a "chip" or integrated circuit (IC)**
 - Small Scale ICs = SSI = ~ 10 gates/chip
 - ✦ AND, OR gates, etc
 - Medium Scale ICs = MSI = ~ 100 gates/chip
 - ✦ Comparators, Multiplexers, Decoders, Adders, ...
 - Large Scale ICs = LSI = ~ 1000-10,000 gates/chip
 - Very Large Scale ICs = VLSI = 100,000+ gates/chip
- **Nowadays, components available in SystemVerilog libraries and FPGA elements**
- **Also useful to discuss functionality of designs**


 


Comparators

Comparator

Carnegie Mellon

  
- **Mission: Compare two inputs**
- **Inputs: unsigned binary numbers**
 - Signed versions also available
- **Outputs: Single bit signals**
 - Is $A = B$?
 - Is $A < B$? Is $A > B$? Available on "Magnitude Comparator"
- **1-bit comparator?**



Multi-bit Comparator

Carnegie Mellon

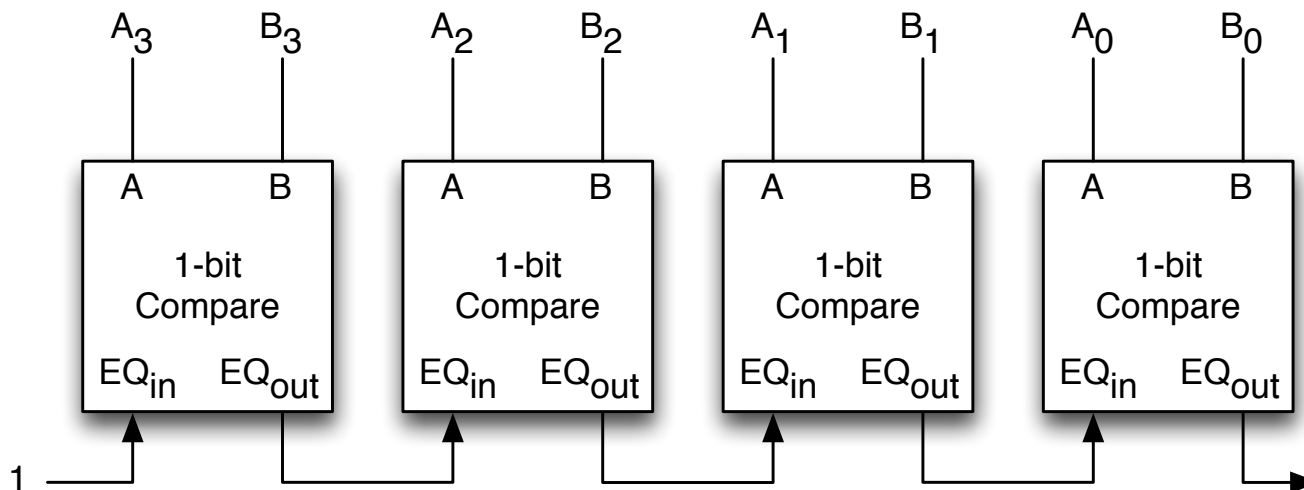
- How do you compare numbers?
- Are these equal? 568743
568941
 - Start at the left and compare digits until you find a difference
- Iterative circuit
 - Repeated use of a basic module with signals cascading



What's in the box?

Carnegie Mellon

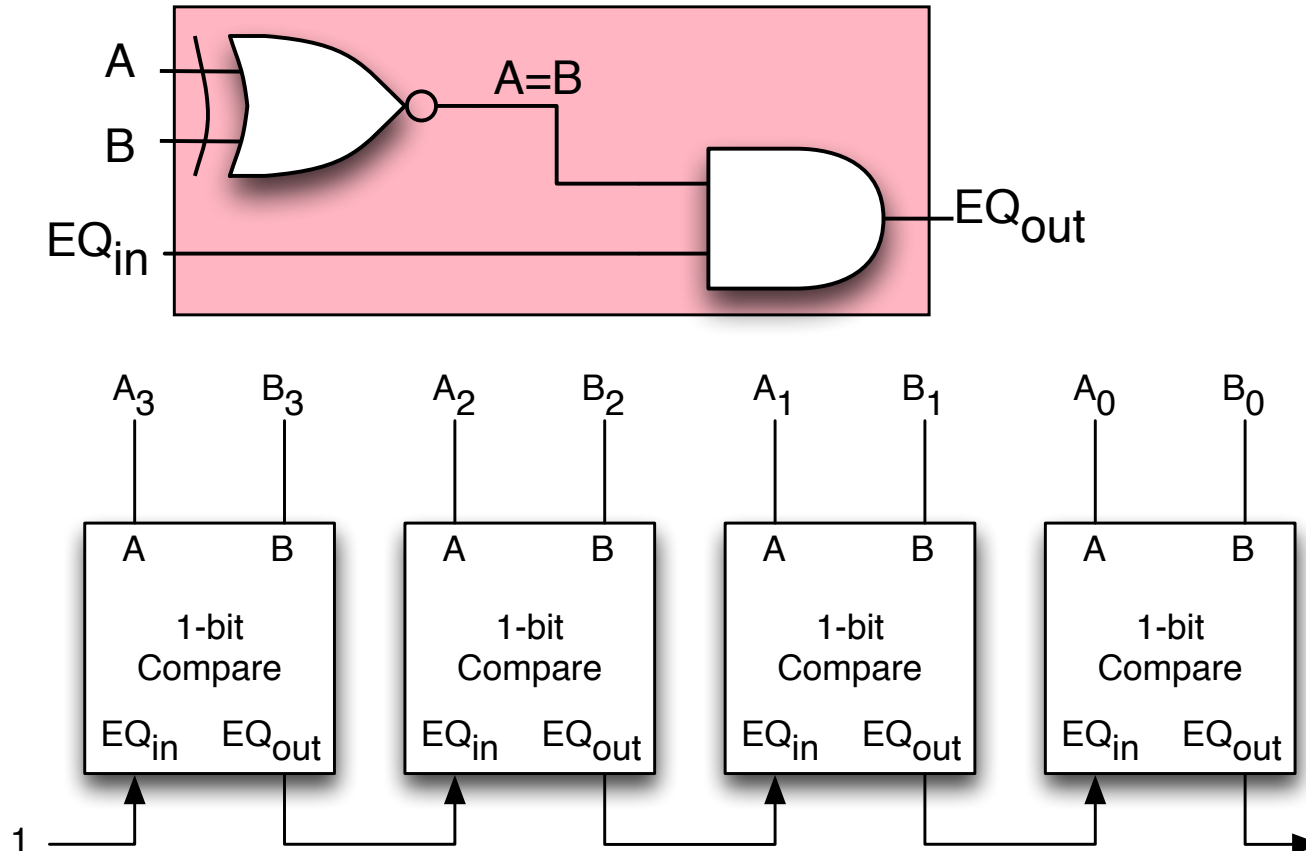- The 1-bit comparison box needs to be able to cascade inputs
 - XNOR isn't good enough
 - $EQ_{out} = 1$ if $(EQ_{in} = 1)$ and $(A = B)$



Multi-bit Magnitude Comparator


Carnegie Mellon

- How do you compare numbers?

- Which is larger? 568743
 568941

- Start at the left and compare digits until you find a difference

AgtB	AEqB	AltB	A	B	AgtB	AeqB	AltB
1	0	0	X	X	1	0	0
0	0	1	X	X	0	0	1
0	1	0	0	0	0	1	0
0	1	0	0	1	0	0	1
0	1	0	1	0	1	0	0
0	1	0	1	1	0	1	0

 

Bit Slicing

- This design method where you solve a problem for one-bit at a time is very useful
- You can replicate the solution n-times for an n-bit circuit
 - No need to re-design / re-solve / re-debug just because you want a 17-bit comparator
- We will see this **bit-slice** design approach in several other circuits, primarily arithmetic

Comparator: SystemVerilog

Carnegie Mellon

- Again, SV operator does this for you

```
module comparator(  
    input  logic [7:0] A, B,  
    output logic      AeqB);  
  
    assign AeqB = (A == B);  
  
endmodule : comparator
```

- Magnitude comparator uses comparison operators


```
assign AltB = (A < B);  
assign AgtB = (A > B);
```

De-multiplexers and Decoders

Demultiplexer: Basic Idea

Carnegie Mellon

 - Opposite of a Mux
- S_1, S_0 select one of 4 outputs to send G to




- What happens to the other 3 outputs?

 Example Use

Carnegie Mellon

- **Telecommunications:** When paired with a Mux, can drastically reduce # wires needed to connect m sources to m receivers




- **Can route data to one of m circuit elements**
 - Often, more efficient to send data to all m circuit elements, and have $m-1$ of them ignore the input

Demux Internals

Carnegie Mellon

 - Each output just needs to check if the select lines apply to it or not




S ₁	S ₀	G	Out ₃	Out ₂	Out ₁	Out ₀
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	0	0
1	1	1	1	0	0	0

Decoder

Carnegie Mellon

 - **Mission: Convert one code to another**
- **Default: Convert binary to "one's hot"**
 - One's Hot: only a single output is 1 ("hot") all other are zero
- **BCD-to-7Segment Decoder is another example that you will see in Lab 2**




I_2	I_1	I_0	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Decoder Internals

Carnegie Mellon

 - How do you build a decoder?
 - Isn't each output active only when the input bits match the code?



- This is a perfectly good, “component-based” way of thinking about building circuits
 - But, it's wrong
 - Too much abstraction, not enough optimization

Decoder Internals, another try

Carnegie Mellon

- Examine the Truth table

I ₂	I ₁	I ₀	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

- What is D₀?


- D₁?

A b-bit decoder is 2^b AND gates, each with b inputs

Decoder Internal Gate Structure

Carnegie Mellon

 - Each output of the decoder is an AND gate connected to some combination of the inputs (and their complemented versions)



Decoder Enable

Carnegie Mellon

- **Enable** on a component lets you control when it should do its job
 - ... and when you want it to shut up


I ₂	I ₁	I ₀	En	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	0	0	0	1	0
0	1	0	1	0	0	0	0	0	1	0	0
0	1	1	1	0	0	0	0	1	0	0	0
1	0	0	1	0	0	0	1	0	0	0	0
1	0	1	1	0	0	1	0	0	0	0	0
1	1	0	1	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0
X	X	X	0	0	0	0	0	0	0	0	0

- Decoder output is always a zero when not enabled

Cascading Decoders

Carnegie Mellon

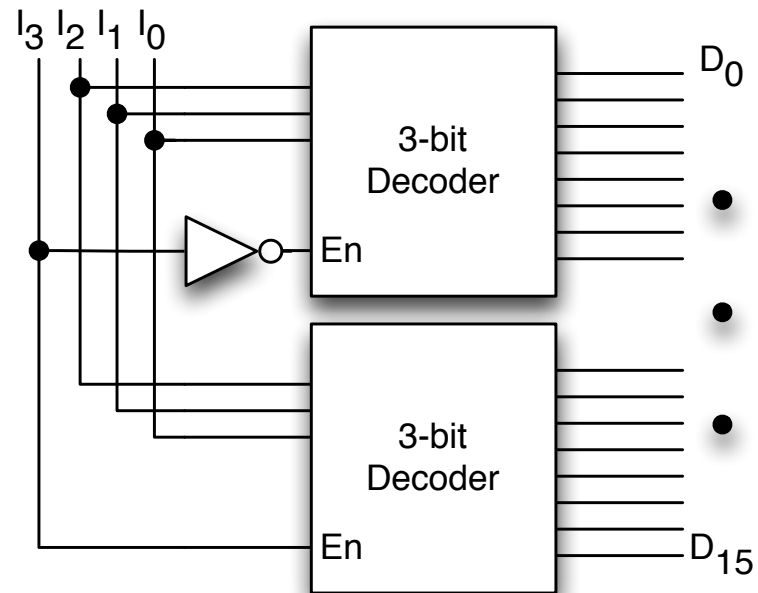- Enable lets you build big decoders out of little ones



Decoder vs. Demux

Carnegie Mellon

- BTW, you've seen Decoder w/Enable before

I ₁	I ₀	En	D ₃	D ₂	D ₁	D ₀
0	0	1	0	0	0	1
0	1	1	0	0	1	0
1	0	1	0	1	0	0
1	1	1	1	0	0	0
X	X	0	0	0	0	0

2-bit Decoder w/Enable

S ₁	S ₀	G	Out ₃	Out ₂	Out ₁	Out ₀
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	0	0
1	1	1	1	0	0	0

2-bit Demultiplexer

Component Summary

Carnegie Mellon

- **Multiplexer (Mux)**
 - Mission: Select an input to put on the output
- **Demultiplexer (Demux)**
 - Mission: Choose an output to get the input
 - Opposite of a Multiplexer (duh, **De**mux)
- **Comparator**
 - Mission: Decide if two multi-bit inputs are the same
 - **Magnitude comparator** also does “less-than” and “greater-than”
 - Bit-slice or "cascade" design technique
- **Decoders**
 - Mission: Convert binary to one-hot code
 - Sometimes convert other codes
 - Some have “enable” input so we can build big from little

Summary

- **Lots of useful components**
 - A standard library of combinational circuits
- **Decoders and Multiplexers are essential components of higher level designs**
 - Computer architecture is littered with them
- **Later in the course, we will find ourselves using these components as building blocks for RTL designs**